

## Exercise 3

Student: *Joshua Feld, 406718*

---

Kurs: *Process Measurement* – Professor: *Prof Dr. Kleinert*

### Task 1. (Strain Gauges)

- a) Describe the working principle of a strain gauge.
- b) Deduce the linear correlation between resistance and length variation.
- c) The figure depicts the circuit diagram of a full bridge circuit. Specify the linearized equation that describes the correlation between measured voltage  $U_m$ , feeding voltage  $U_s$  and the resistors  $R_i$  ( $i = 1, \dots, 4$ ).
- d) For the purpose of this task, assume that the depicted full bridge circuit is attached to a carrier for bending measurements. Determine the impact of temperature changes within the resistors on the measured voltage  $U_m$ .

**Lösung.**

### Task 2. (Capacitive Displacement Measurement)

The structural setup of a capacitive displacement measurement, which includes three capacitor plates, is depicted in the figure below. Specify the formula for the determination of  $x$ . Assume that the capacity is given.

**Lösung.**